

## Complexity Theory

### WS 2011/2012, Exercise Sheet #9

#### EXERCISE 24:

The lecture has considered Boolean circuits composed from binary AND and OR and unary NOT.

- a) Let us now temporarily permit AND and OR gates with an unbounded number of inputs, the *size* of such a gate being this number. Prove: In every circuit of polynomial (why?) size, these gates can be replaced by their binary counterparts while the size grows at most by a constant factor and depth by at most a logarithmic one.
- b) Now demonstrate that the three above types of gates can be replaced by one single type to rebuild all circuits while affecting both depth and size by no more than a constant factor.
- c) Prove that, from AND and OR alone, only *monotone* functions can be realized, i.e. satisfying
$$\forall 1 \leq j \leq n \quad \forall x_1, \dots, x_n: \quad f(x_1, \dots, x_{j-1}, 0, x_{j+1}, \dots, x_n) \leq f(x_1, \dots, x_{j-1}, 1, x_{j+1}, \dots, x_n) .$$
- d) Recall Exercise 9g) and prove: Every language  $L \subseteq \{0, 1\}^*$  can be decided by a family of circuits of circuits. What size and depth do you achieve? Is the family uniform?
- e) The Boolean function  $\text{Mux}_n : (x_1, \dots, x_n; y_0, \dots, y_{2^n-1}) \mapsto y_{(x_1, \dots, x_n)_2}$  is called a **Multiplexer**. Sketch a circuit  $C_n$  for  $\text{Mux}_n$  of depth  $\mathcal{O}(n)$ . Is  $(C_n)_n$  uniform?

#### EXERCISE 25:

Fix  $\Gamma \subseteq \{0, 1\}^k$  and  $Q \subseteq \{0, 1\}^\ell$  and  $\delta : \Gamma \times Q \mapsto \Gamma \times Q \times \{00, 01, 10\}$ .

- a) Describe a circuit  $C_\delta$  computing  $\delta$ .
- b) Let  $\mathcal{M} = (Q, \Sigma, \Gamma, \delta)$  denote a DTM and  $s \in \mathbb{N}$ . Describe a circuit  $C'_{\delta, s}$  with the following functionality:  
Its input consists of the encoding of a configuration of  $\mathcal{M}$ : state, tape contents of length  $\leq s$  with one bit per cell indicating whether the head is presently reading it. The output of  $C'_{\delta, s}$  encodes  $\mathcal{M}$ 's configuration one step later, that is, the new state, new tape contents with updated indicators for the head position.  
How large and deep is  $C'_{\delta, s}$ , depending on  $s$ ?
- c) Let  $n \in \mathbb{N}$ ,  $s \geq S_{\mathcal{M}}(n)$ , and  $t \geq T_{\mathcal{M}}(n)$ . Describe a circuit  $C'_{\mathcal{M}, s, t}$  simulating  $\mathcal{M}$  on all inputs of length  $n$ . Estimate the size and depth of  $C'_{\mathcal{M}, s, t}$  asymptotically in terms of  $s$  and  $t$ .
- d) Prove that a polynomial-time DTM  $\mathcal{M}$  can be simulated by a uniform family of polynomial size circuits. Moreover, CIRCUITVAL is  $\mathcal{P}$ -complete.